

## Compressor/Limiter/Clipper for FM broadcasting

### Why is it important to use this device?

Audio signals as music or speech have big dynamic ranges. There are silent and loud sections. These audio signals aren't too good for a transmitter, which requires audio signal with constant level on the input. Limiter is a device, which weakens loud signals and intensifies silent signals. On its output there is signal with constant level. Signal clipping on the limiter output allows to increase the signal level without exceeding maximum frequency deviation limit 75 kHz. It's very suitable since preemphasis is used.



If your transmission chain does not include any similar device, you should build this one. You will be surprised by its quality, efficiency and simplicity. This is the Pira CZ Compressor/Limiter/Clipper.

Be careful if you want to buy any simple compressor/limiter board available on the market! Although a big list of features is mentioned, some of these toys have no signal overshooting protection and have no precise preemphasis with HF clipping option. With these devices it's not possible to keep loud sound AND meet the frequency deviation limit. So there is no reason why to pay for them. The device should guarantee basic technical characteristics of the modulation signal, nothing more - no equalizers and other disutilities.


### Characteristics:

- Absolutely no signal overshooting (tested with [PIRA75 FM Broadcast Analyzer](#))
- Low noise and distortion
- Simple to adjust
- Only a few parts to solder

- Precise preemphasis including HF clipping with no distortion audible
- Stereo version available [here](#)

Supply voltage: 9-16 V  
 Quiescent supply current (12 V): 15 mA  
 Output voltage: linear adjustable 0-3.5 V p-p (0-1.2 V rms)  
 Lower cut-off frequency (3 dB): input: 25 Hz, output: <2 Hz  
 Upper cut-off frequency (3 dB): 14.5 kHz  
 Min. input voltage: 0.6 V p-p (0.2 V rms)  
 Input impedance: 5000 ohm  
 Output impedance: 500 ohm  
 Signal-to-noise ratio: >70 dB

**Schematic diagram:**

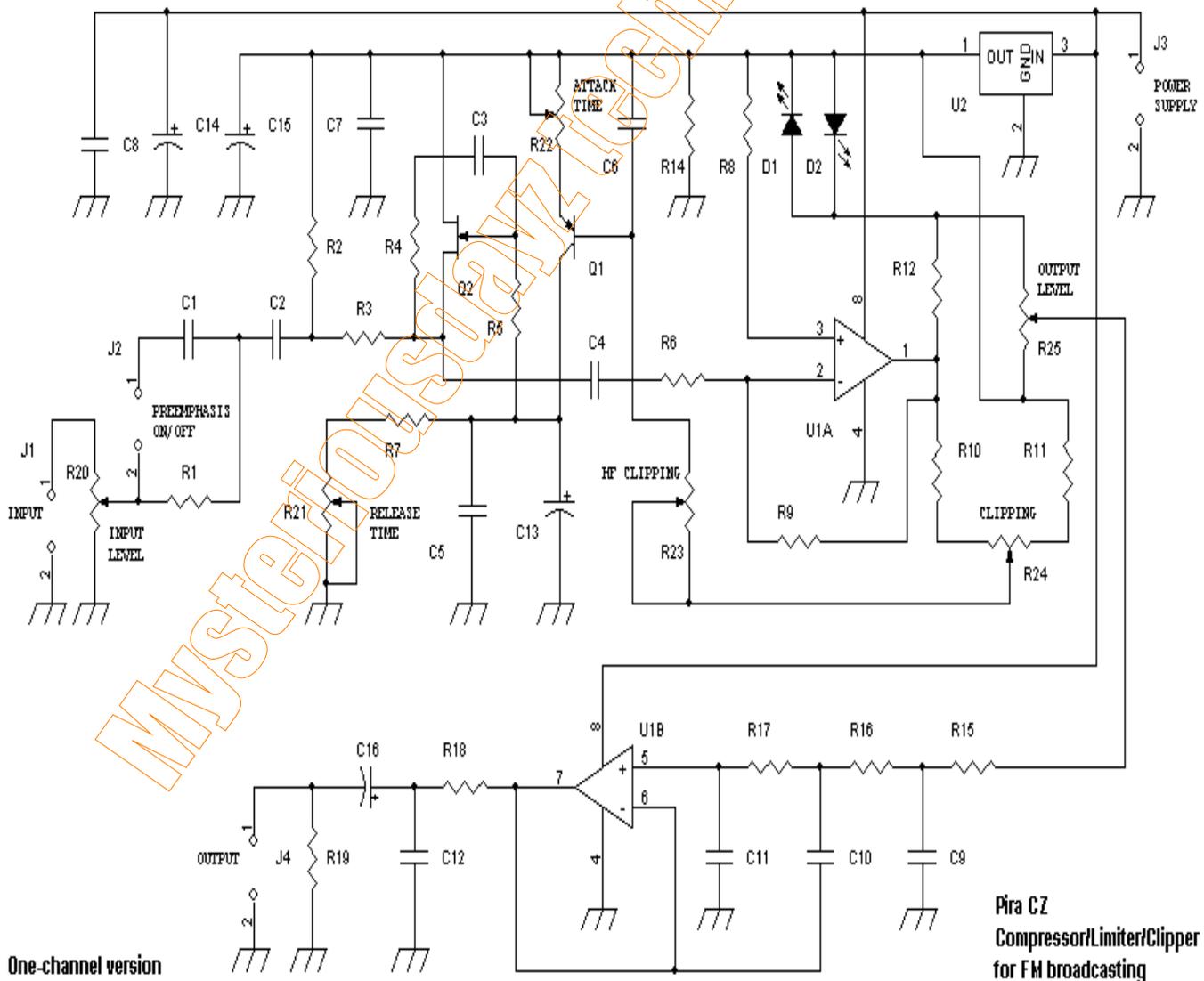

### Part list:

R1, R3 - 10k  
R2 - 1k  
R4, R5 - 1M  
R6 - 18k  
R7, R8, R15-R17, R19 - 33k  
R9 - 1M5  
R10, R12, R14, R18 - 470R  
R11 - 270R  
R20, R23, R25 - trimmer 5k  
R21 - trimmer 5M  
R22 - trimmer 1k  
R24 - trimmer 500R

C1 - 4n7 (EU) or 6n8 (USA), plastic  
C2 - 470n plastic  
C3 - 4n7 plastic  
C4 - 330n plastic  
C5, C7, C8, C12 - 10n ceramic  
C6 - 22n ceramic  
C9 - 330p ceramic  
C10 - 470p ceramic  
C11 - 82p ceramic  
C13 - 10u/25V tantalum  
C14 - 470u/25V electrolytic  
C15, C16 - 220u/10V electrolytic

U1 - TLC272  
U2 - 78L05  
Q1 - BC557B  
Q2 - BF245C  
D1, D2 - **Red!!!** LED diode 5 mm, medium luminance (eg. 200 mcd)  
J2 - jumper


### Adjusting elements description:

Preemphasis on/off - Connect (close) the jumper to turn on the preemphasis - recommended just here.

Attack time, release time - Compressor/limiter time constants. The attack time should usually be as small as possible, the release time determines the signal processing intensity.

Clipping, HF clipping - Recommended adjustment procedure: 1) Set the HF clipping to the middle, set the Clipping closely below clipping level of low frequencies (1 kHz and lower). 2) Adjust HF clipping on a common program content. Check the sibilancy (hiss) reproduction - no distortion should be audible. The more clipping the more signal loudness.

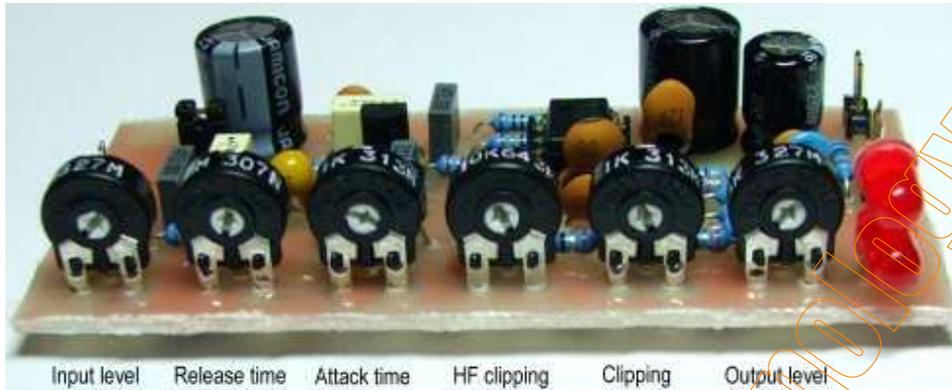Input level - Gate function analogy. If set right, background sound (noise, hum) present in original signal is not amplified and clipping is working on all common program content.



Two LED diodes indicate the clipping. Very short peaks clipping may not be visible.

Mysteriousdayz technology